



ON Semiconductor®

Switcher Efficiency & Snubber Design

Agenda


- SMPS Basics
- Control Methods
- Losses
- Example: Buck
- Example: Boost
- BJTs vs. MOSFETs
- Snubber Design



SMPS Basics




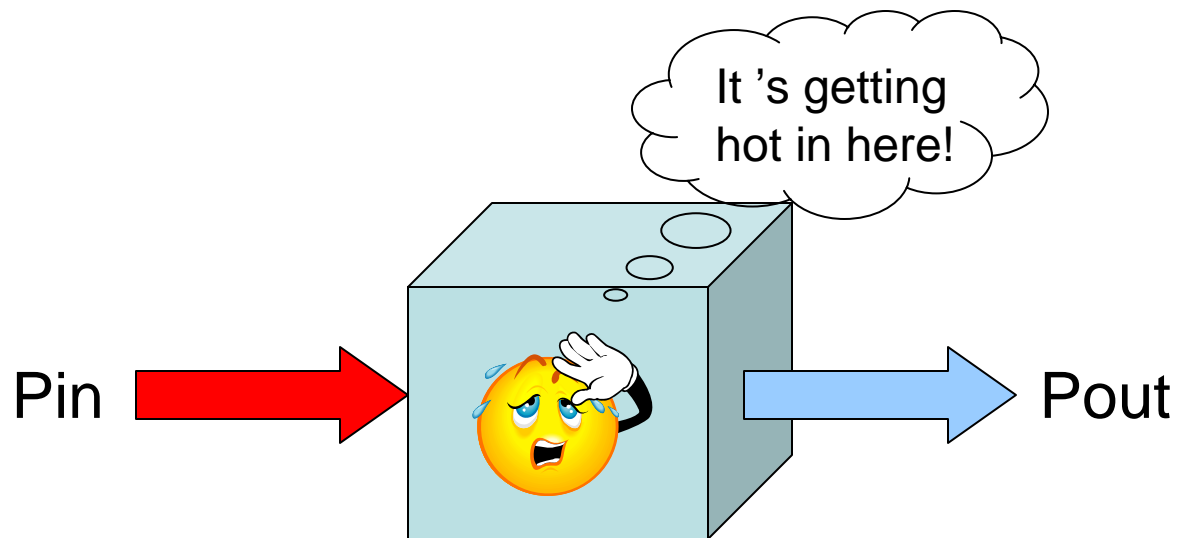The goal of a converter is to deliver power



The conversion mechanism generates heat...

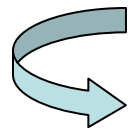Heat means that the energy transfer is **not** perfect



$\eta = P_{out}/P_{in}$ is called the efficiency

$$P_{loss} = P_{in} - P_{out} = \frac{P_{out}}{\eta} - P_{out} = P_{out} \cdot \left(\frac{1}{\eta} - 1 \right)$$



A 50% efficiency means $P_{loss} = P_{out}$

e.g. $P_{out} = 100 \text{ W} \rightarrow P_{loss} = 100 \text{ W}$


$P_{in} = 150 \text{ W}, P_{out} = 100 \text{ W} \rightarrow \eta = 66\%$

Two different options exist to build a converter:




The **linear** approach:

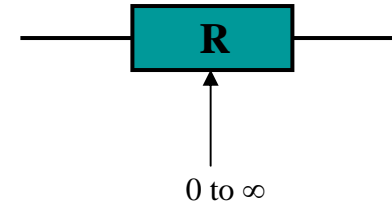- efficiency is poor
- good noise performance
- acceptable when $(V_{out}-V_{in})$ is small
- can only decrease the input level




The **switching** approach:

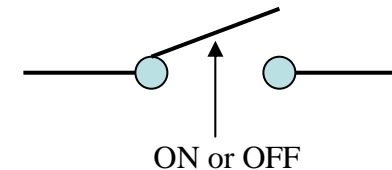
- efficiency is high
- noise performance is poor
- works with large $(V_{out}-V_{in})$
- increase/decrease/invert the input level



The *linear* approach:

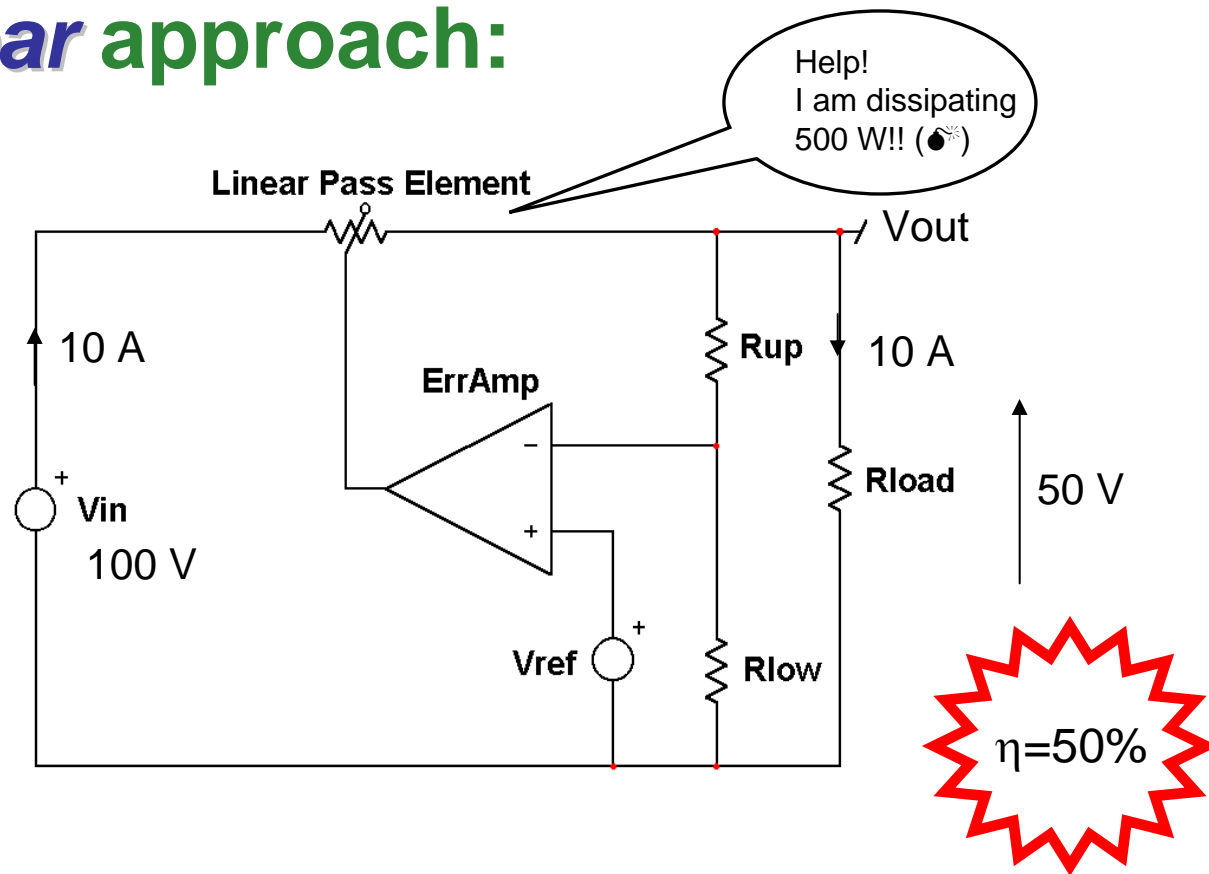


The *switching* approach:

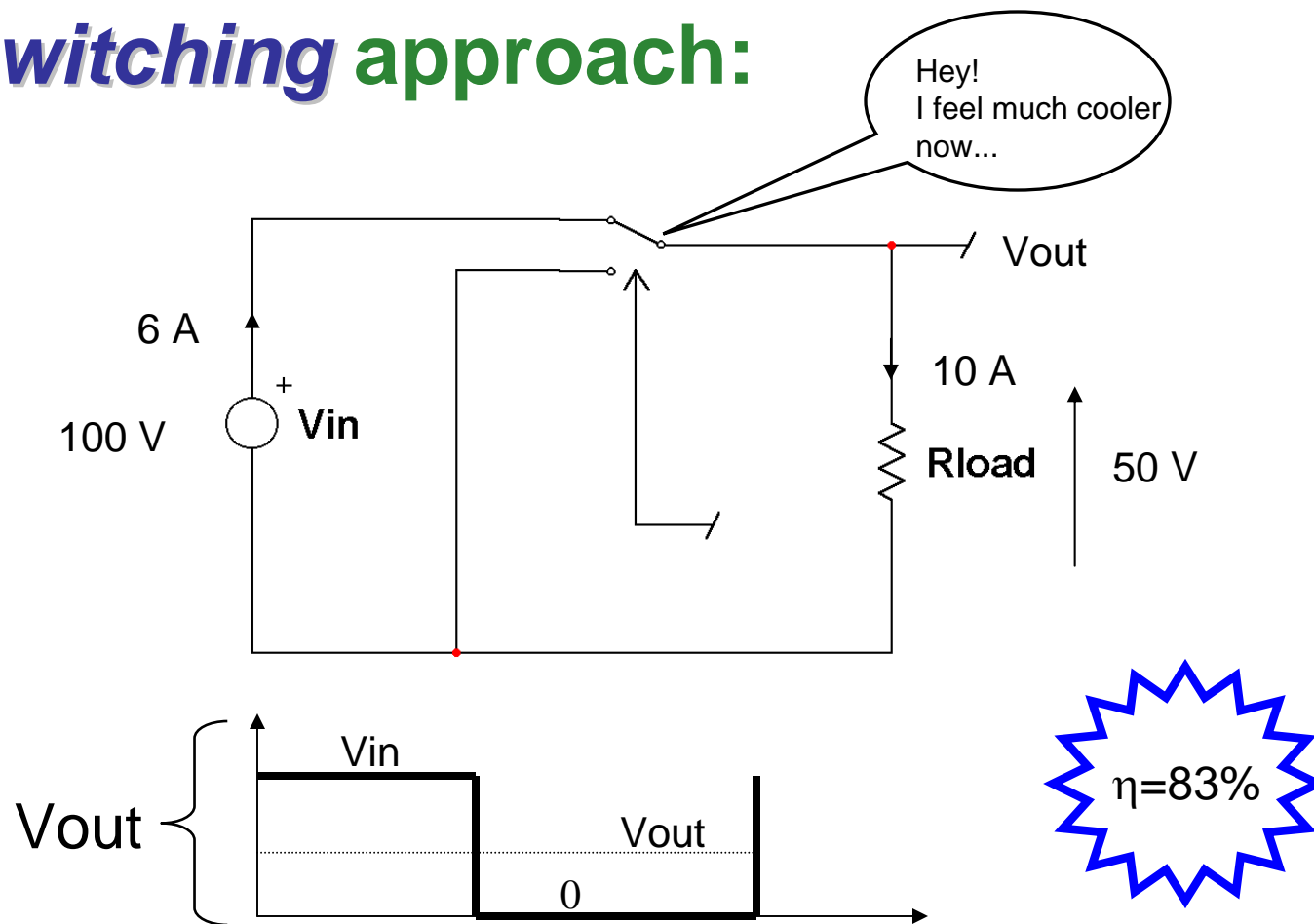


Controlling the power flow
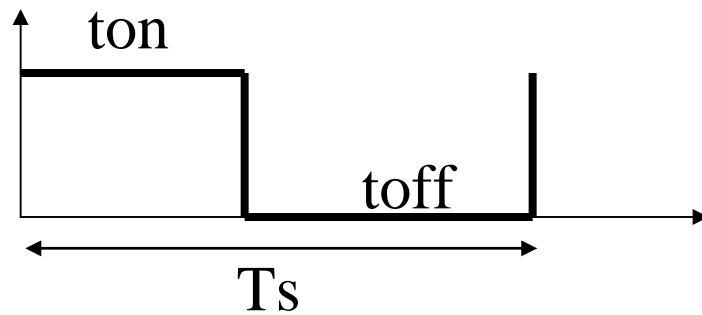
$$V_{out_{avg}} = \frac{1}{T_s} \cdot \int_0^{T_s} V_{out}(t) \cdot dt = \frac{ton}{T_s} \cdot V_{in} = D \cdot V_{in}$$


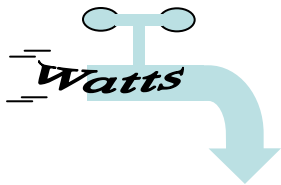
$$D = \frac{ton}{T_s} \text{ (Duty-cycle)}$$



➡ **Pulse Width Modulation (PWM) control**

Control Methods



Regulation, keeping an output signal constant by...


- adjusting the **duty-cycle** via the PWM block
- regulating the inductor **peak** current
 - regulating the inductor **average** current
 - adjusting the **switching** frequency
 - **off** time adjustment
 - ...

Current-mode control...

Voltage-mode control...


} Two most popular methods!

The voltage-mode method

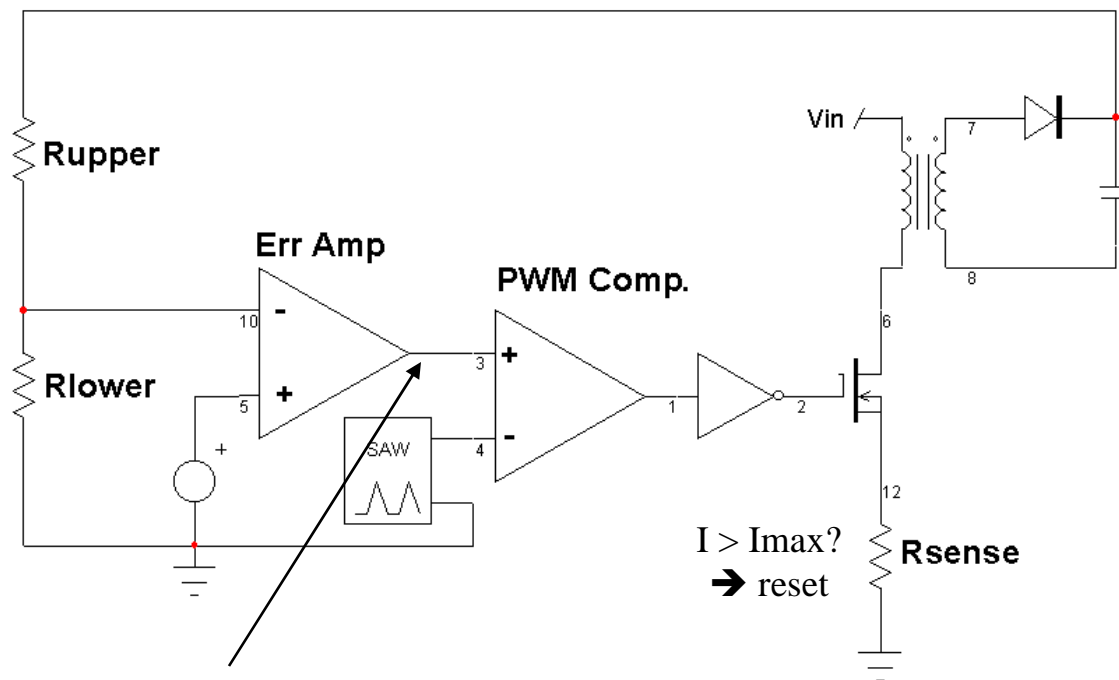


The error level sets the duty-cycle

The duty-cycle factory...

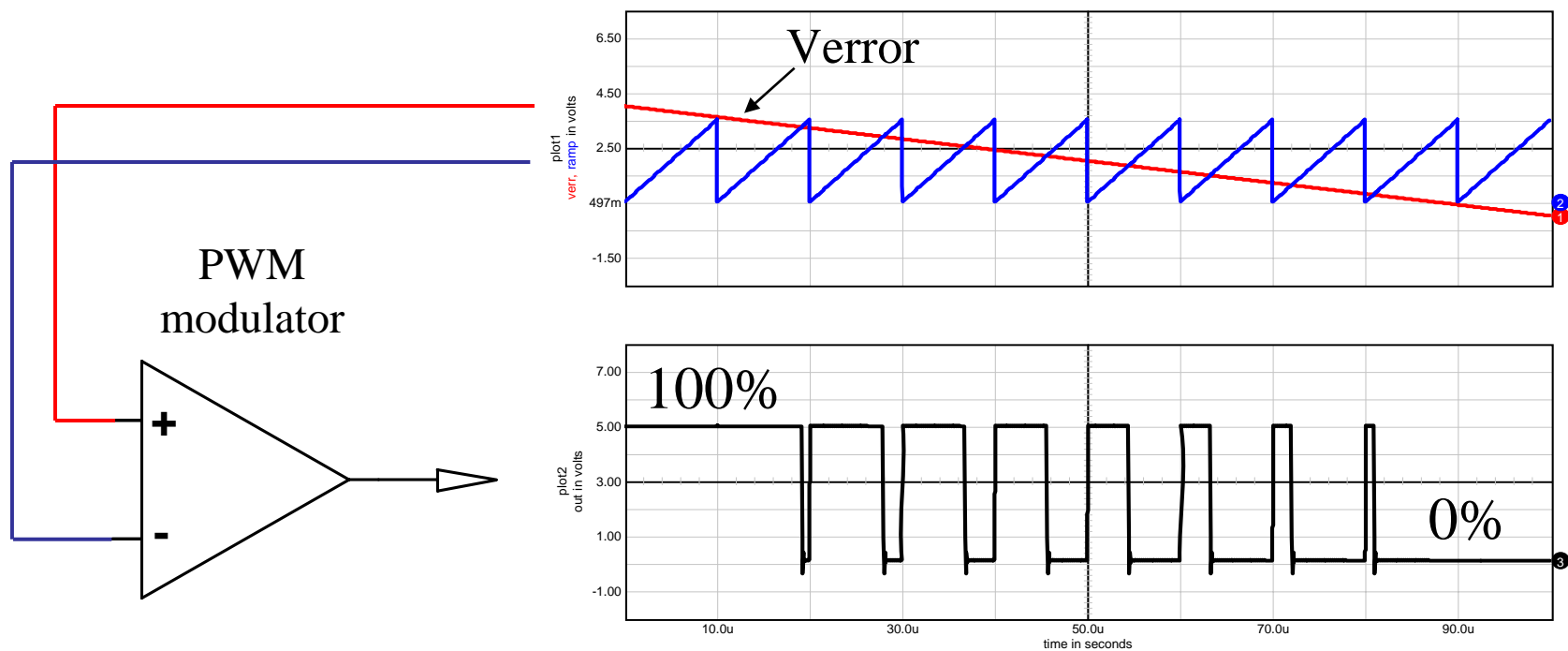


A ramp is compared to a DC level, the error voltage

The current-mode method

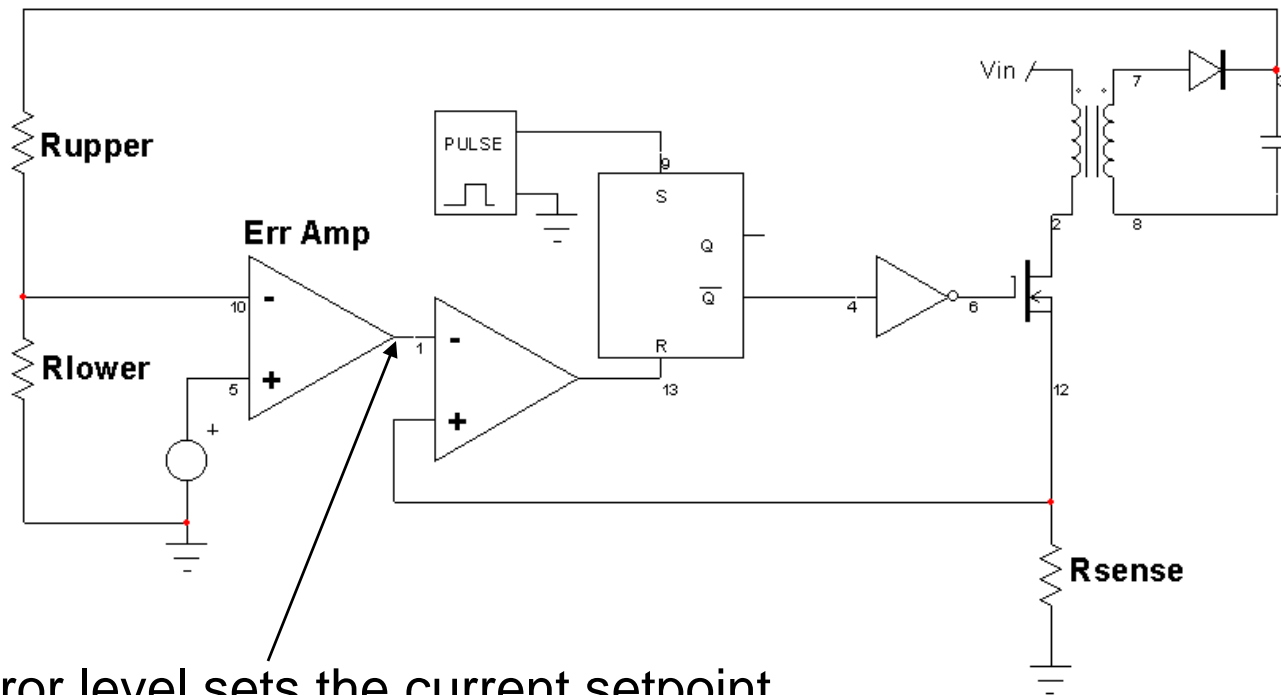

The error level sets the current setpoint

The peak follows the error voltage

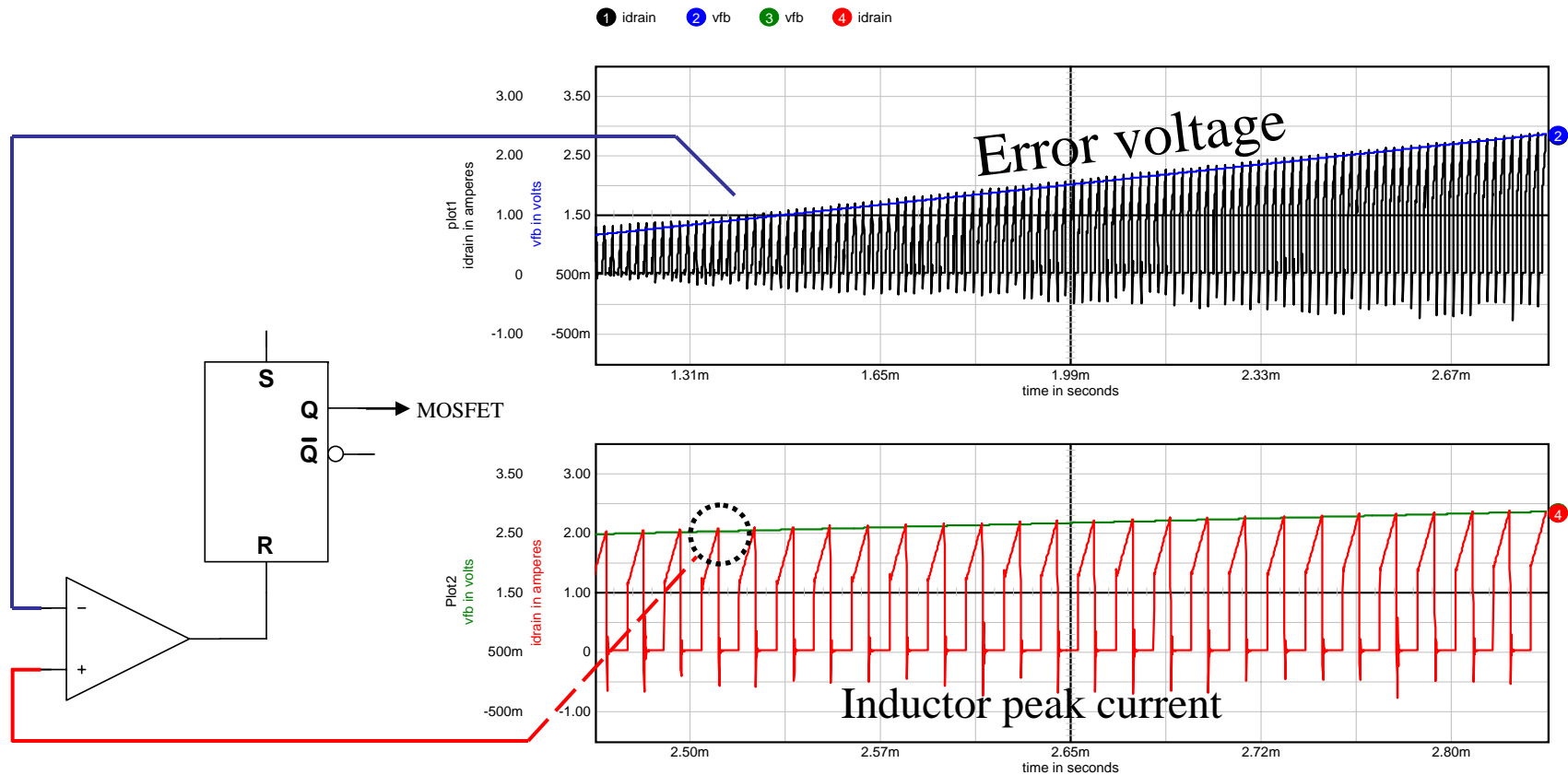

Losses



Losses

$$P_{out} = P_{in} - P_{SW} - P_{Con} - P_{IC}$$

P_{SW} : Switching Losses

P_{Con} : Conduction Losses

P_{IC} : Power consumed by the chip



IC Losses


$$P_{IC} = V_{in} I_q$$

V_{in}: IC input voltage

I_q: Quiescent current (read from the data sheet)

Switching Losses

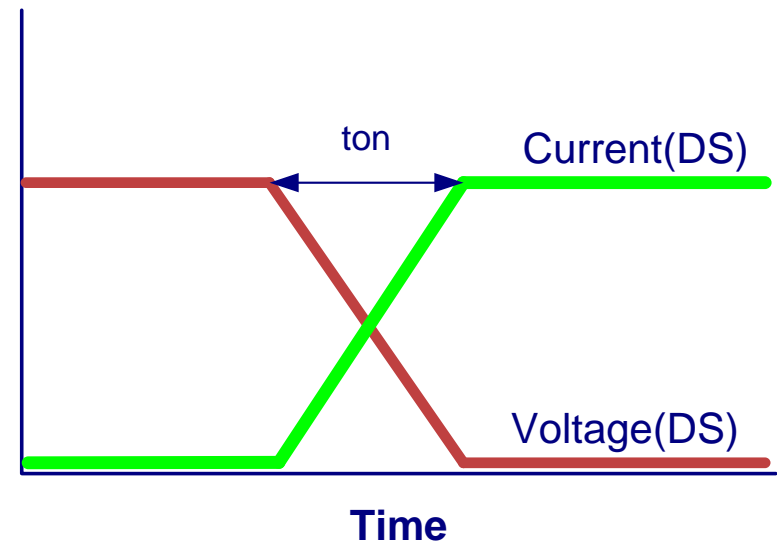- Losses which occur when the power switch is turned on or off.
- During this transition the voltage and current on the FET are both high.
- Different for Buck and Boost configurations.



Switching Losses (Buck)

$$P_{SW} = \frac{1}{2} V_{in} I_{out} (t_{on} + t_{off}) F_{SW}$$

V_{in} : Input Voltage

I_{out} : Average inductor current

t_{on} : Turn on time of high side switch

t_{off} : Turn off time of high side switch

F_{SW} : Switching frequency

Switching Losses (Boost)

$$P_{SW} = \frac{1}{2} V_{out} \frac{I_{out}}{1-D} (t_{on} + t_{off}) F_{SW}$$

V_{out} : Output Voltage

D : Duty Cycle

I_{out} : Average inductor current

t_{on} : Turn on time of high side switch

t_{off} : Turn off time of high side switch

F_{SW} : Switching frequency

Reducing Switching Losses

- Increase gate drive strength
 - Increases cost (die area)
 - Increases EM emissions
- Decrease frequency
 - Requires a larger value inductor
- Use a smaller FET
 - Increases conduction losses



Conduction Losses

- Losses which occur when current flows through a resistive path ($I^2 \cdot R$), such as a FET, or a diode ($V \cdot I$).
- Major contributors include:
 - Power Switch $R_{ds,on}$
 - Freewheeling Diode
 - Inductor DCR
- Different for synchronous and non-synchronous mode designs.

Conduction Losses (Non-Synchronous)

$$P_{Con} = I_L^2 R_{ds,on} D + I_L V_{diode} (1 - D) + I_L^2 R_{DCR}$$

I_L : RMS current through the inductor

$R_{ds,on}$: On resistance of the power switch

D : Duty cycle

V_{diode} : Forward voltage of the diode

R_{DCR} : Winding resistance of the inductor

Conduction Losses (Synchronous)

$$P_{Con} = I_L^2 R_{ds,on1} D + I_L^2 R_{ds,on2} (1 - D) + I_L^2 R_{DCR}$$

I_L : RMS current through the inductor

$R_{ds,on1}$: On resistance of the high side switch

D : Duty cycle

$R_{ds,on2}$: On resistance of the low side switch

R_{DCR} : Winding resistance of the inductor

Example: Buck



Example: NCV8851 Evaluation Board

- Synchronous buck converter
- $V_{in} = 13.2 \text{ V}$
- $V_{out} = 5 \text{ V}$
- $I_{out,max} = 4 \text{ A}$
- $F_{SW} = 170 \text{ kHz}$
- Inductor: Würth Electronics 7447709150 15 μH
- Power switch (both): ON Semiconductor NTD5407N




Example: NCV8851 Evaluation Board

- $D = V_{in} / V_{out} = 5 \text{ V} / 13.2 \text{ V} = 0.379$
- $t_{on} = 5 \text{ ns}$ (empirical)
- $t_{off} = 7 \text{ ns}$ (empirical)
- $R_{ds,on1} = R_{ds,on2} = 50 \text{ m}\Omega$ (including self heating temperature effects)
- $R_{DCR} = 26 \text{ m}\Omega$
- $I_q = 15 \text{ mA}$
- $I_L = \text{Sqrt}(I_{out}^2 + (0.609 \text{ A})^2 / 3)$

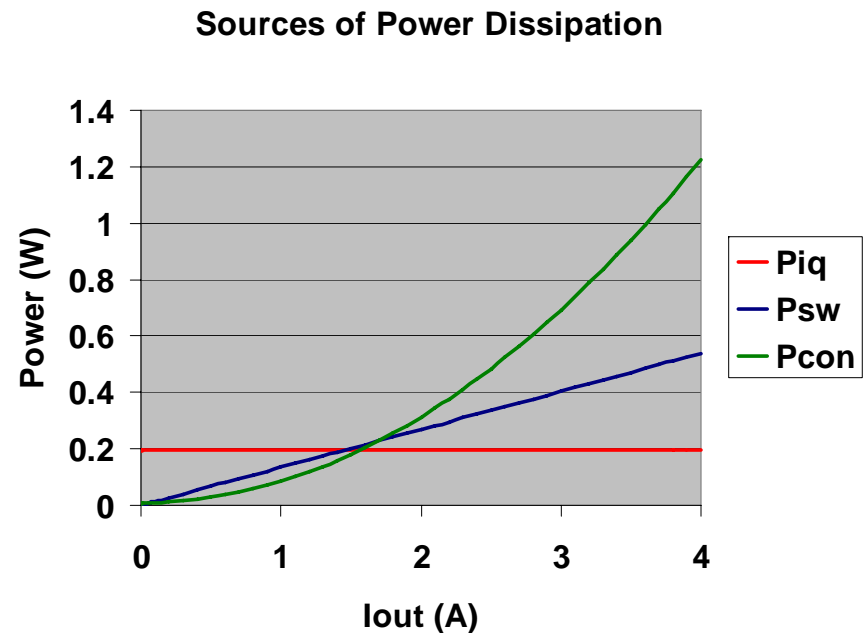
Example: NCV8851 Evaluation Board

- $P_{IC} = 13.2 \text{ V} * 15 \text{ mA}$
 $= \mathbf{0.198 \text{ W}}$
- $P_{SW} = (1/2) * 13.2 \text{ V} * I_{out} * (5 \text{ ns} + 7 \text{ ns}) * 170 \text{ kHz}$
 $= \mathbf{0.01346 * I_{out} \text{ W}}$
- $P_{CON} = (I_{out}^2 + 0.12378 \text{ A}^2) * (50 \text{ m}\Omega) * (0.379) + (I_{out}^2 + 0.12378 \text{ A}^2) * (50 \text{ m}\Omega) * (0.621) + (I_{out}^2 + 0.12378 \text{ A}^2) * 26 \text{ m}\Omega = \mathbf{(0.076 * I_{out}^2 + 0.009407) \text{ W}}$



Example: NCV8851 Results

8851 Efficiency

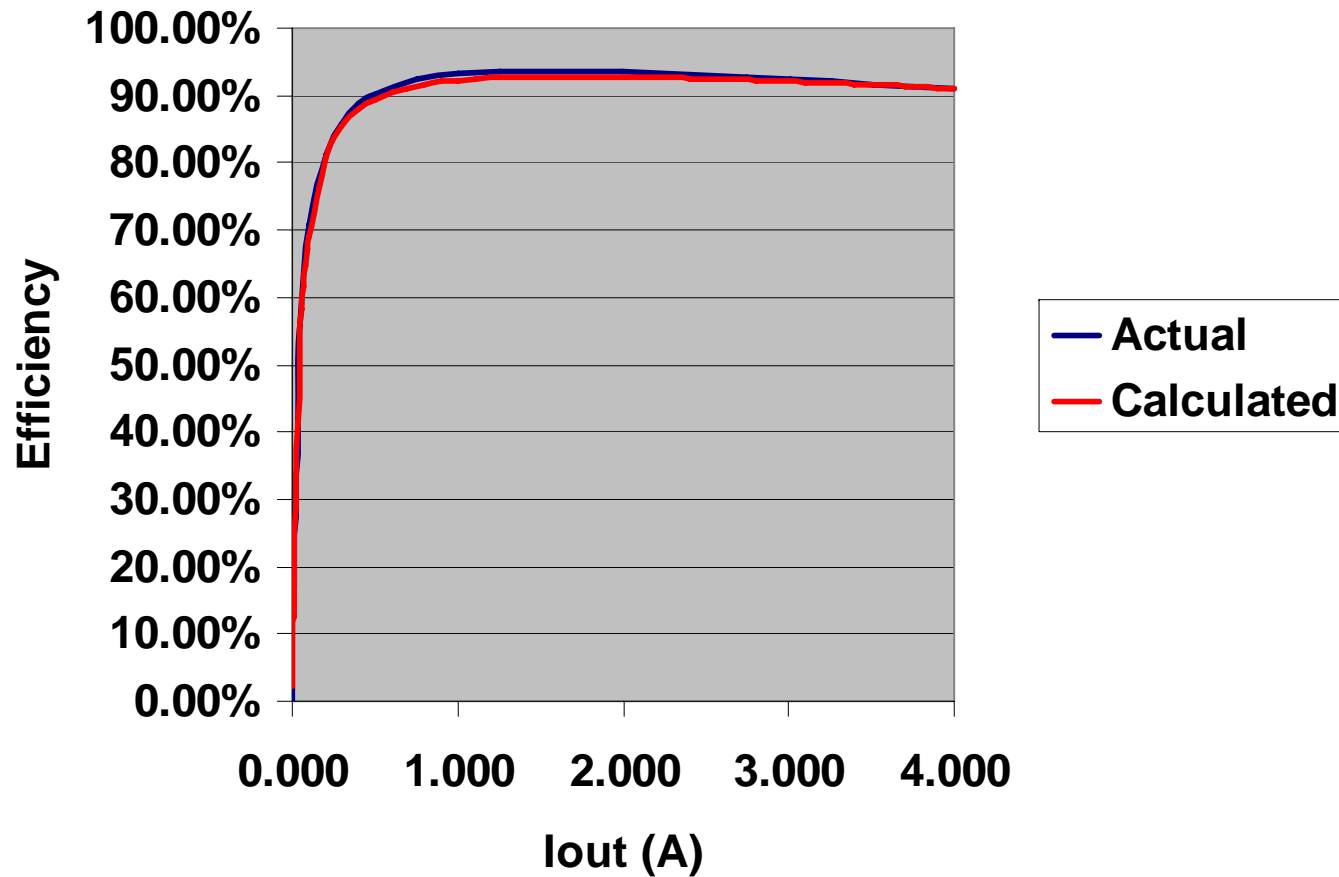

Example: Boost



Example: NCV8871 Sample Application


- Non-synchronous boost converter
- $V_{in} = 13.2 \text{ V}$
- $V_{out} = 18 \text{ V}$
- $I_{out,max} = 9 \text{ A}$
- $F_{SW} = 170 \text{ kHz}$
- Inductor: Vishay IHLP6767GZER330M11 33 μH
- Power Switch: ON Semiconductor NTD5803 x 2
- Diode: ON Semiconductor MBRB1645T4G

Example: NCV8871 Sample Application


- $D = 1 - (V_{in} / V_{out}) = 0.267$
- $t_{on} = 30 \text{ ns}$
- $t_{off} = 20 \text{ ns}$
- $R_{ds,on} = (12 \text{ m}\Omega) / 2 = 6 \text{ m}\Omega$ (including temperature effects)
- $R_{DCR} = 37 \text{ m}\Omega$
- $I_q = 10 \text{ mA}$
- $IL = \text{Sqrt} ((I_{out} / (1 - D))^2 + (0.3137)^2 / 3)$

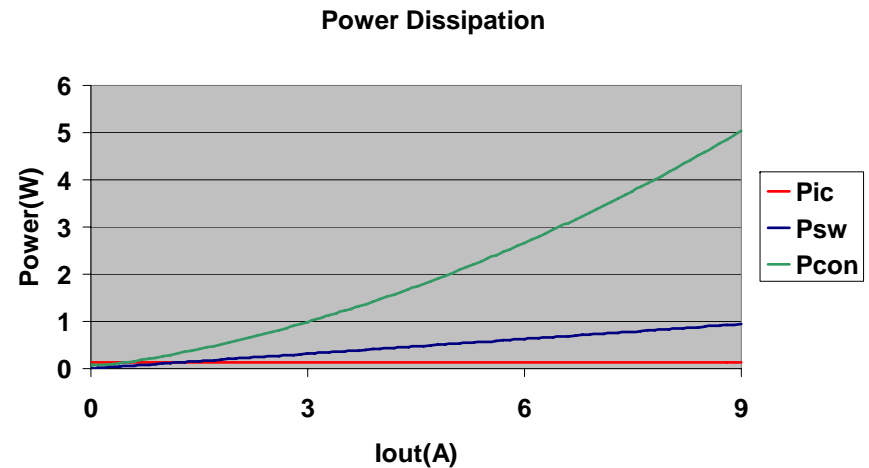Example: NCV8871 Sample Application

- $P_{IC} = 13.2 \text{ V} * 10 \text{ mA} = \mathbf{0.132 \text{ W}}$
- $P_{SW} = (1/2) * 18 \text{ V} * I_{out} / (1-0.267) * (20 \text{ ns} + 30 \text{ ns}) * 170 \text{ kHz} = \mathbf{0.10436 * I_{out} \text{ W}}$
- $P_{CON} = (I_{out}^2 + 0.0328 \text{ A}^2) * (12 \text{ m}\Omega) * (0.267) + \text{Sqrt}(I_{out}^2 + 0.0328 \text{ A}^2) * (0.5 \text{ V}) * (0.733) + (I_{out}^2 + 0.0328 \text{ A}^2) * 37 \text{ m}\Omega = \mathbf{(0.0402 * I_{out}^2 + \text{Sqrt}(I_{out}^2 + 0.0328) * 0.3665 + 0.00131869 \text{ W})}$



Example: NCV8871 Results

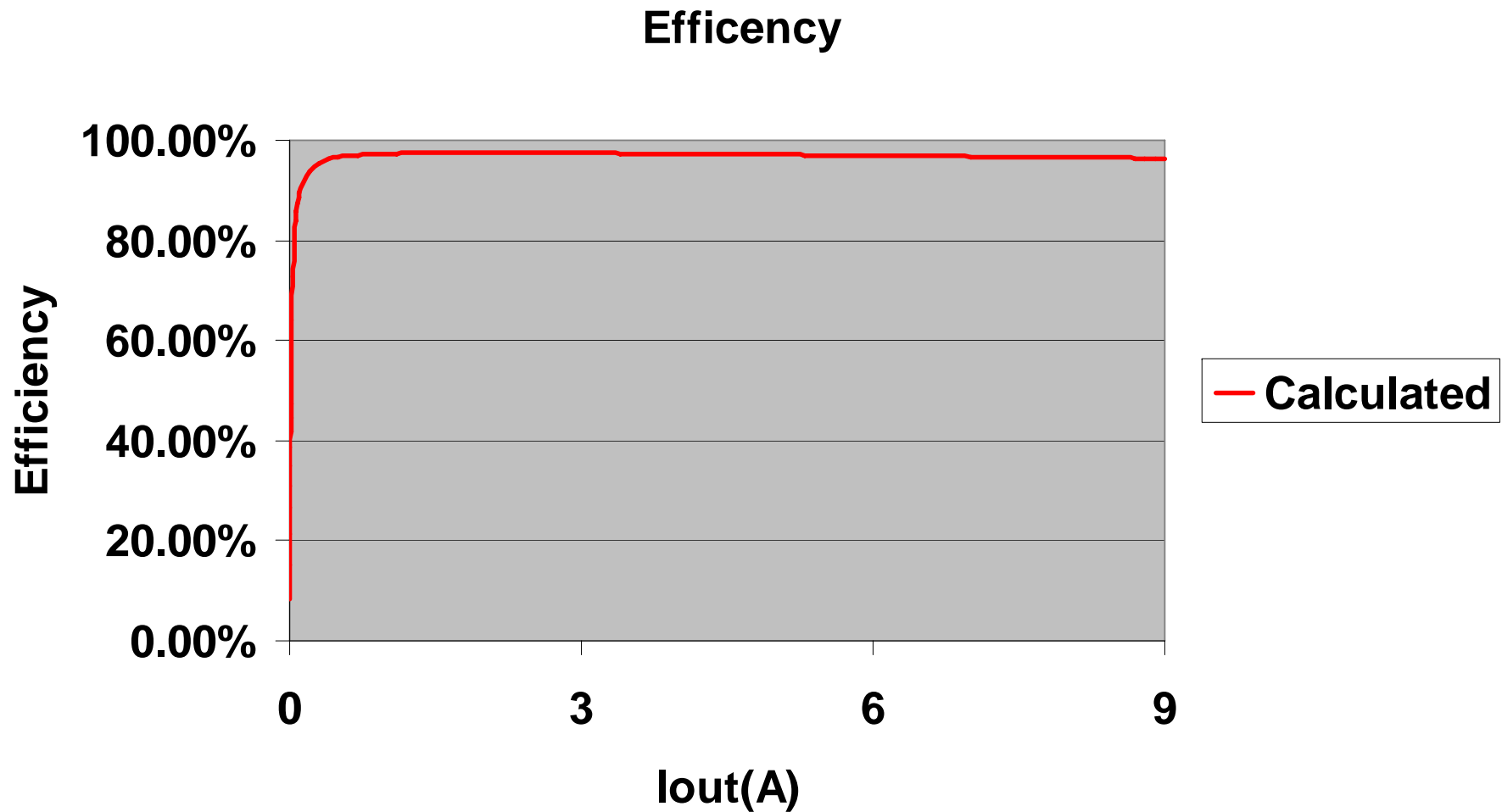


BJTs vs. MOSFETs



Switches and converters...

- ❑ The bipolar transistor is often used:
 1. In high voltage - high current applications
 2. In low-cost converters

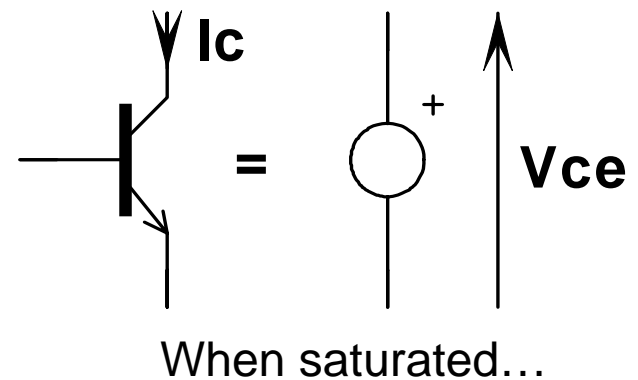
➡ $P_{cond} = V_{ce_{sat}} \cdot I_{c_{avg}}$



The bipolar transistor

Switches and converters...

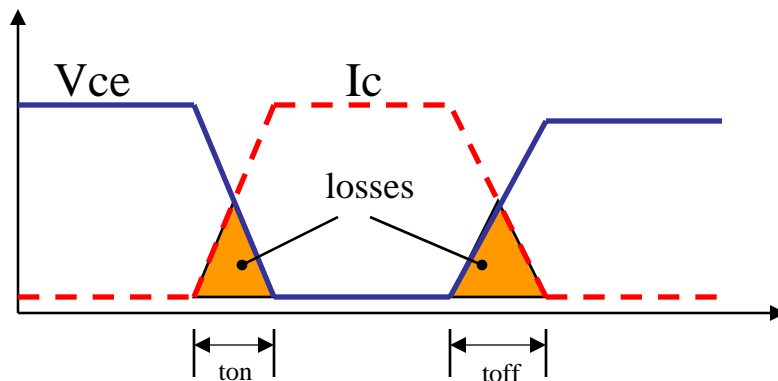- ❑ The bipolar transistor switching losses:
 1. Depend on temperature (storage time, current tail)
 2. Watch-out for hot spots!
 3. Often needs proportional drive (shallow saturation)




$$P_{sw} = \frac{V_{ce} \cdot I_c \cdot (t_{on} + t_{off})}{3 \cdot T_{sw}} \quad \text{If } t_{on} = t_{off} \dots$$

The bipolar transistor

Switches and converters...



- ❑ The MOSFET transistor is the most popular:
 1. Ease of drive (capacitive input)
 2. Avalanche rugged
 3. BVdss of 600 V for SMPS, 500 V for PFCs...

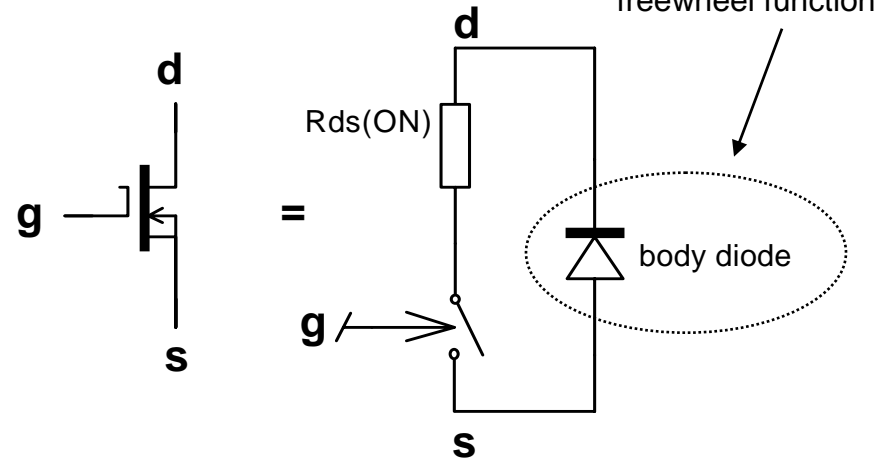➡ $P_{cond} = I_{dRMS}^2 \cdot R_{ds(ON)}$



The MOSFET transistor

To enhance a MOSFET, bring it charge

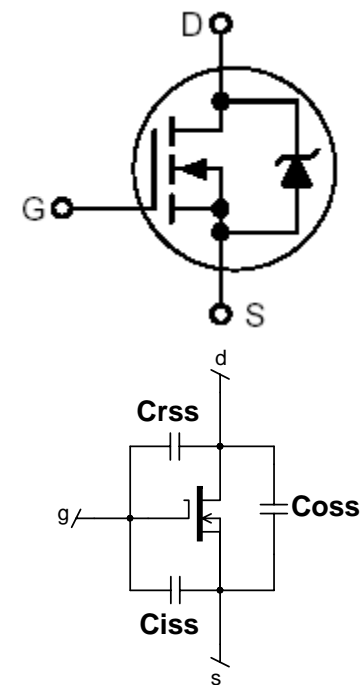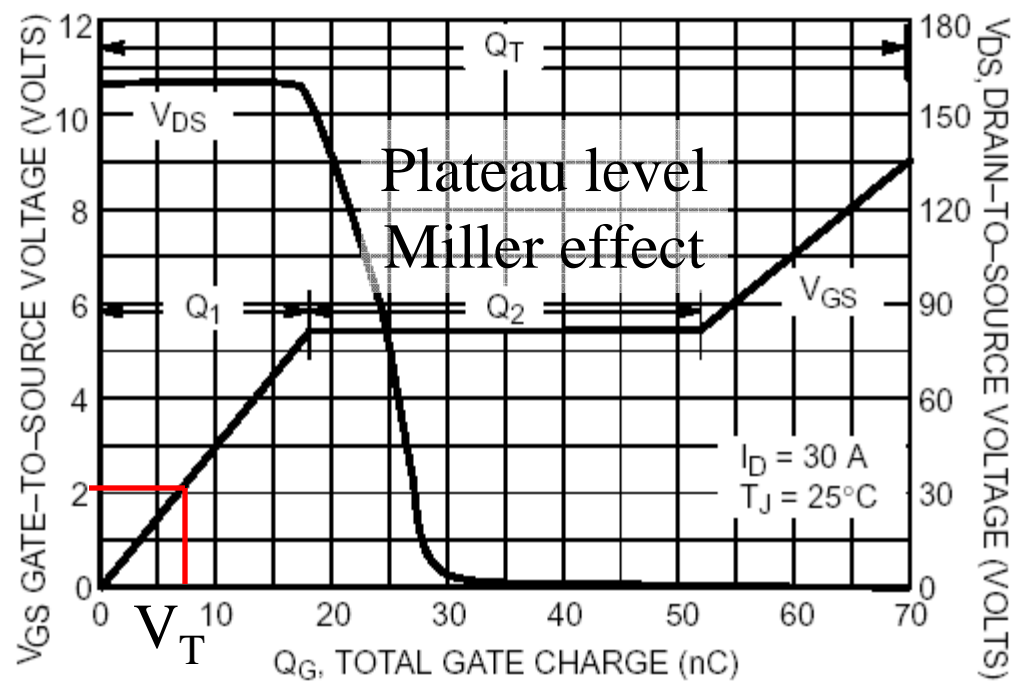


How many coulombs to turn on the MOSFET: $Q = i \times t \dots$

Snubber Design



When is it needed?

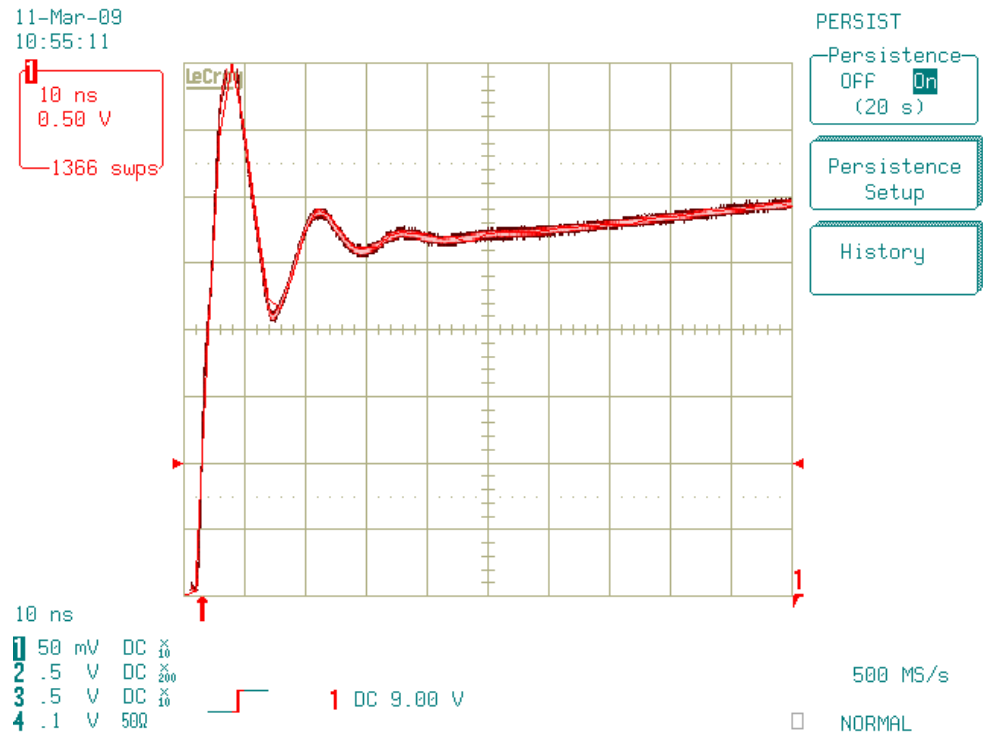- Parasitic inductances and capacitances from the power devices form a RLC filter that resonates
- Excessive ringing can cause damage to the devices



Snubber Design

- Measure the frequency of the ringing (f_c) at maximum input voltage
 - Use a low capacitance probe
- Find out either the L or C of the circuit
 - L is dominated by the top power switch
 - C is dominated by the body diode of the bottom power switch or the capacitance of the freewheeling diode
- Calculate the characteristic impedance of the circuit
 - If L is known: $Z = 2\pi f_c L$
 - If C is known: $Z = 1 / (2 \pi f_c C)$



Snubber Design

- Choose $R_{\text{SNUB}} = Z$
- Choose $C_{\text{SNUB}} = 1 / (2 \pi f R)$
- Power dissipation in R_{SNUB} is CV^2f_s
- Put R_{SNUB} and C_{SNUB} in series across the device causing ringing.
- Test in circuit. R_{SNUB} can be fine tuned further to reduce ringing if it is found to be insufficient

For More Information

- View the extensive portfolio of power management products from ON Semiconductor at www.onsemi.com
- View reference designs, design notes, and other material supporting automotive applications at www.onsemi.com/automotive

